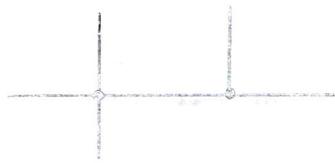


Wire Symbols



Ground Symbols



Experiment - 1

Aim: To study different types of electrical symbols.

Component name.

Meaning


Wire symbols

- Electrical wire - Conductor of electric current.
- Connected wire - Connected crossing
- Not connected wire - Wires are not connected



Ground symbols

- Earth Ground - Used for zero potential reference and electrical shock protection
- Chassis Ground - Connected to the chassis of the circuit
- Digital/Common ground

Resistor symbols

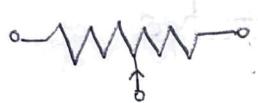

Capacitor symbols

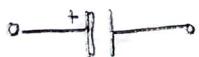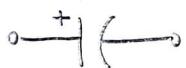

Inductor | Coil symbols



Component NameMeaningResistor symbol

- Resistor (IEE)
- Resistor (IEC)
- Potentiometer (IEEE)
 - Resistor reduces current flow
 - Adjustable resistor
 - has 3 terminals

Capacitor symbol




- Capacitor
 - Capacitor is used to store electric charge. It acts as short circuit with AC open circuit with DC
- Polarized capacitor
 - Electrolytic Capacitor
- Polarized capacitor
 - Electrolytic capacitor
- Variable capacitor
 - Adjustable capacitance

Inductor / Coil symbols

- Inductor
 - Coil / solenoid that generates magnetic field



Power Supply Symbols

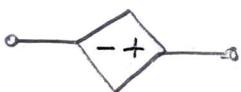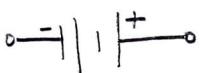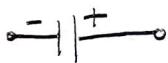


<u>Component name</u>	<u>meaning</u>
-----------------------	----------------

- Iron Core inductor - Includes iron
- Variable Inductor

<u>Power Supply symbols</u>

- Voltage Source - Generates constant voltage
- Current source - Generates constant current
- AC Voltage Source - AC Voltage Source
- Generator - Electrical voltage is generated by mechanical rotation of the generator
- Battery cell - Generate constant voltage
- Battery - generate constant voltage
- Controlled voltage source - Generate voltage as a function of voltage or current of other circuit element
- Controlled current source - Generate current as a function of voltage.

Meter symbols

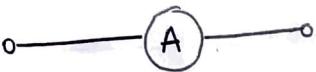

Lamp / Light bulb symbols



Diode / LED symbols



Component NameMeaningMeter symbols

- Voltmeter - Measures voltage. Has very high resistance. Connected in parallel.
- Ammeter - Measures electric current. Has near zero resistance. Connected serially.
- Ohmmeter - Measures resistance
- Wattmeter - Measures electric power.

Lamp/light bulb symbols


- Lamp/ Light bulb
- Lamp/ light bulb - Generates light when current flows through
- Lamp light bulb

Diode / LED symbols

- Diode - Diode allows current in



MISC Symbols

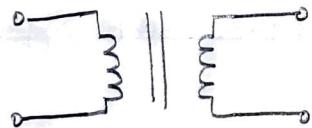

Component Name.Meaning

one direction only (L to R)

- Zener diode
 - Allow current flow in one direction, but also can flow in the reverse direction when above breakdown voltage.
- Light Emitting Diode (LED)
 - LED emits light when current flows through.
- Photodiode
 - Photodiode allows current flow when exposed to light

Misc. Symbols

- Motor
 - Electric motor
- Transformer
 - Change AC voltage from high to low or low to high.
- Electric bell
 - Rings when activated
- Buzzer
 - Produces buzzing sound.



Antenna Symbols



<u>Component Name</u>	<u>Meaning</u>
• Fuse	- The fuse disconnects when current above threshold. Used to protect circuit from high currents.
• fuse	

Antenna Symbols

- Antenna / aerial - Transmits & receives radio waves.
- Antenna / aerial

Experiment - 2

Aim - To study connection of lamp key

- 1) Single way switch
- 2) Two way switch


Apparatus - lamps with holders, connecting wires, one way ~~to~~ two way switches, etc

Theory-

One way - A one way lighting circuit is a simple circuit that enables one circuit to be turned on or off with one switch. The single circuit may have one or more lights in it. This type of circuit uses a one way switch.

Two way - A two way lighting circuit enables one circuit to be turned on or off by either of two switches. The circuit may have one or more lights in it. This type of circuit uses two of the two way switches.

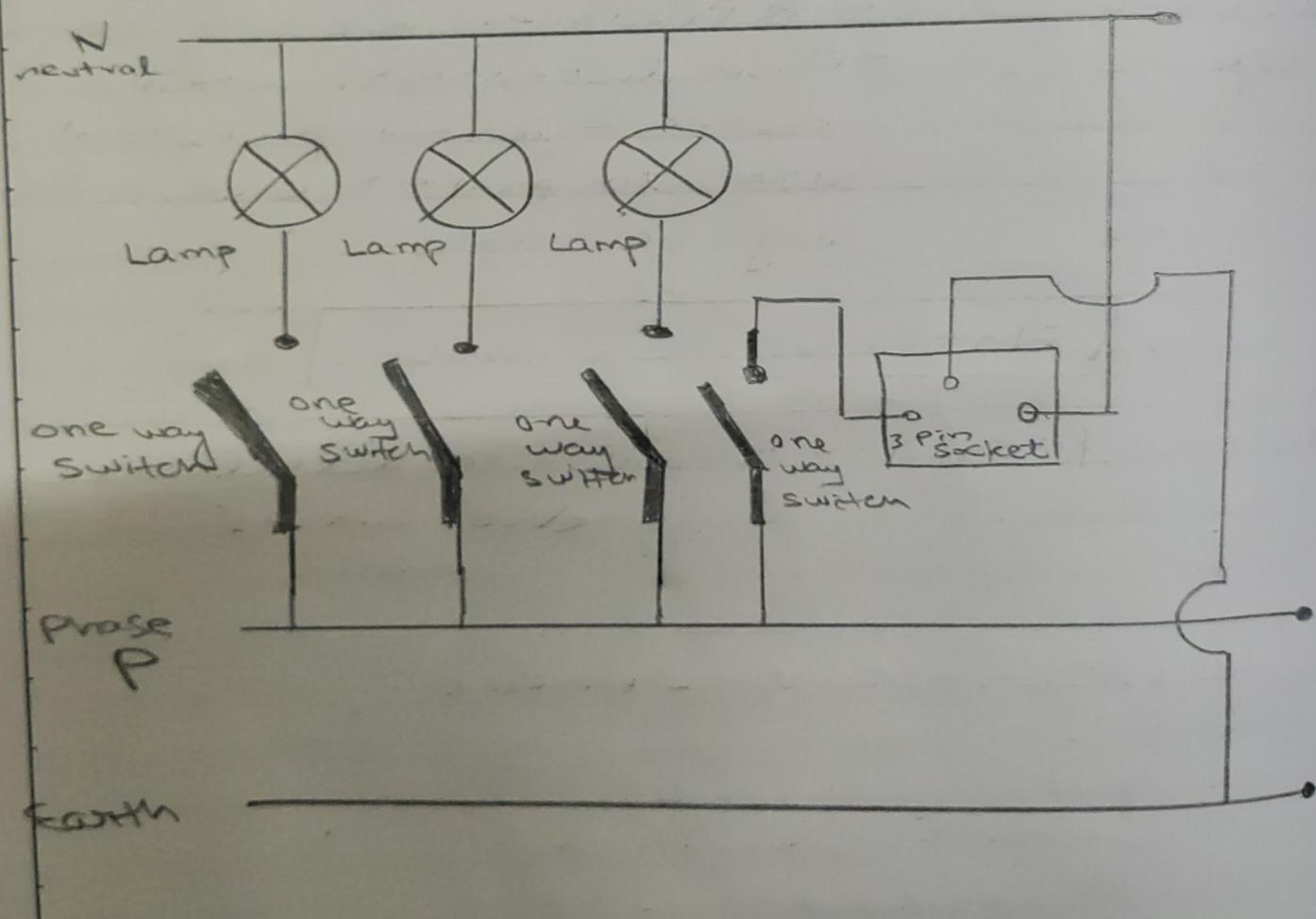Two way switching means having two or more switches in diff. locations to control the lamp. They are wired so that operation of either switch will control the light. The arrangement is often found in stairways, with one switch upstairs & one switch downstairs, or in long hallways with a



switch at either end.

Here we have a schematic (fig 1) which makes it easy to visualize how this circuit works. In this state the lamp is off, changing the position of either switch will switch the live to the lamp turning it on as shown in (fig 2). If you now change the position of the other switch the circuit is broken once again.

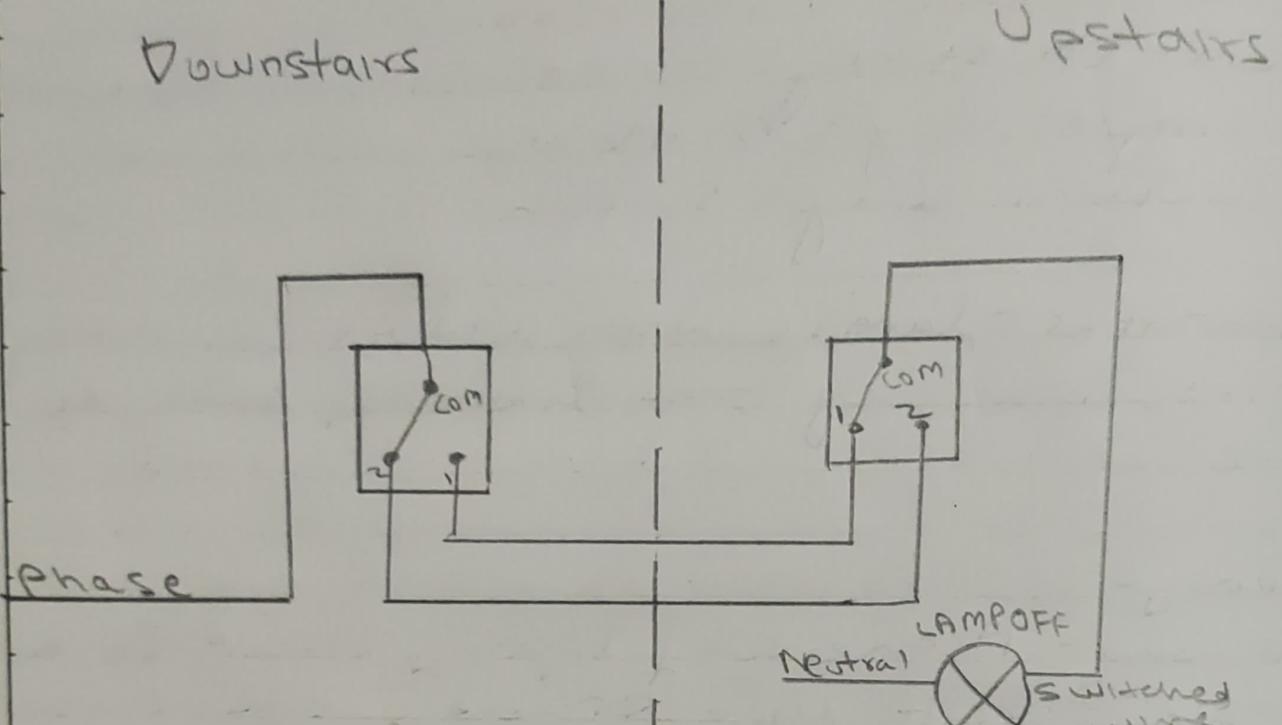


Figure 1

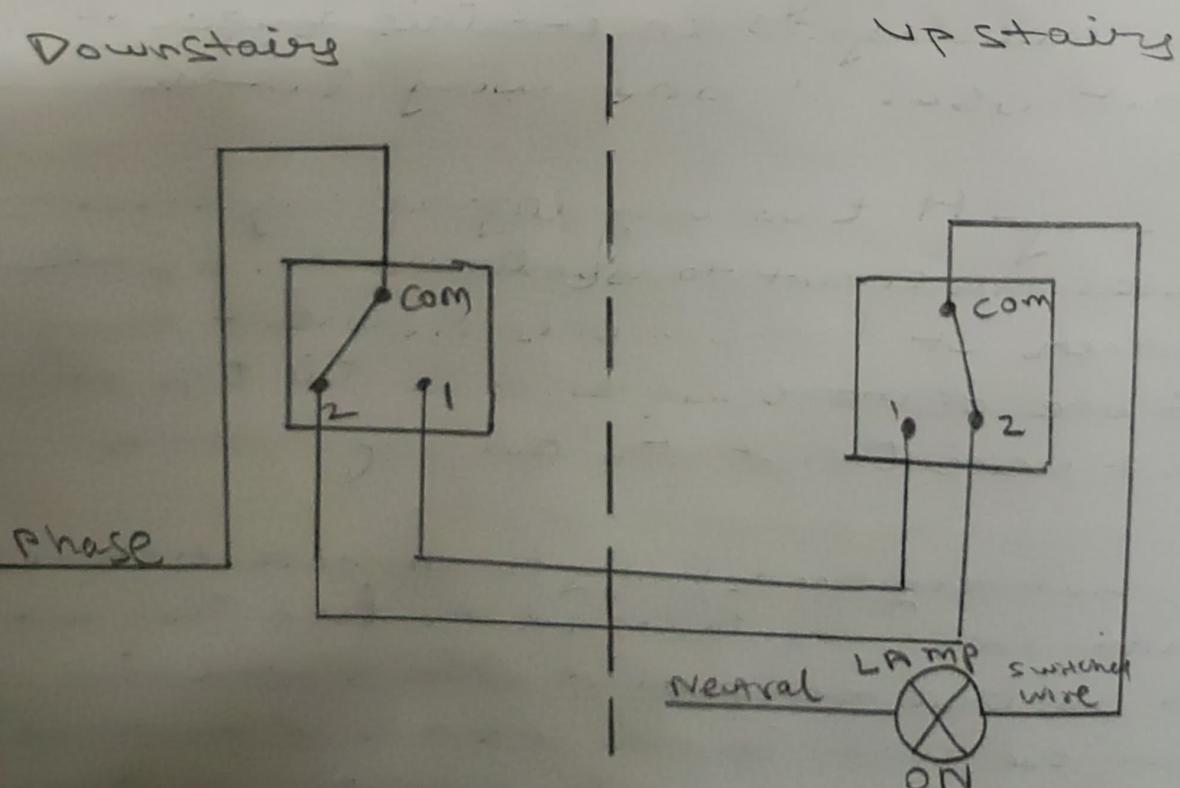


Figure 2

EXPERIMENT NO. 3

AIM: To verify thevenin & Norton's theorem

THEORY

THEVENIN'S THEOREM

The I flowing through a R_L connected across any two terminals A and B of a linear, active bilateral network is given by $V_{oc} / (R_{th} + R_L)$ where V_{oc} is the open circuit voltage known as Thevenin's voltage (V_{th}) and R_{th} is the internal resistance known as Thevenin's resistance of the network as viewed back into the open circuited network from terminals A and B with all voltage source replaced by their internal resistance (short circuit) & I sources by ∞ resistance (open circuit).

PROCEDURE: THEVENIN'S THEOREM

1. Apply a D.C. voltage from voltage source to the input terminals of the network & the output voltage V_{oc} (V_{th}) without load.
2. Connect the load at the output of the network & measure the current I_L through the load.
3. Disconnect the voltage source & load, short the input terminals of the network & measures the thevenin's equivalent resistance at the output terminals.
4. Draw the thevenin equivalent circuits by connecting R_{th} in series with V_{th} .
5. Adjust the input voltage of the voltage source that equals

Teacher's Signature.....

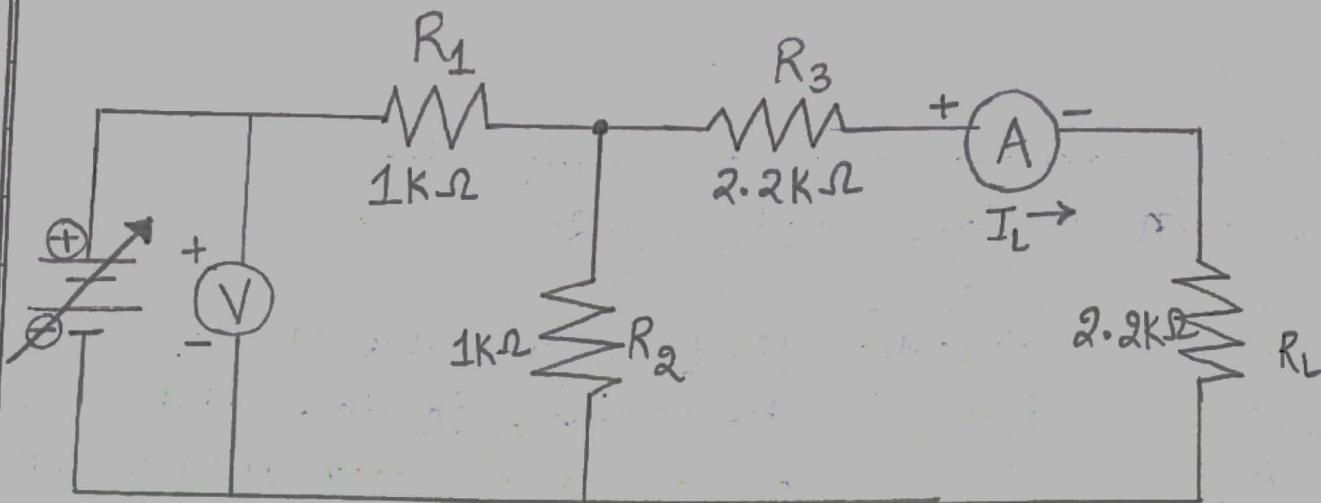


Fig 3-a Circuit is theveninised


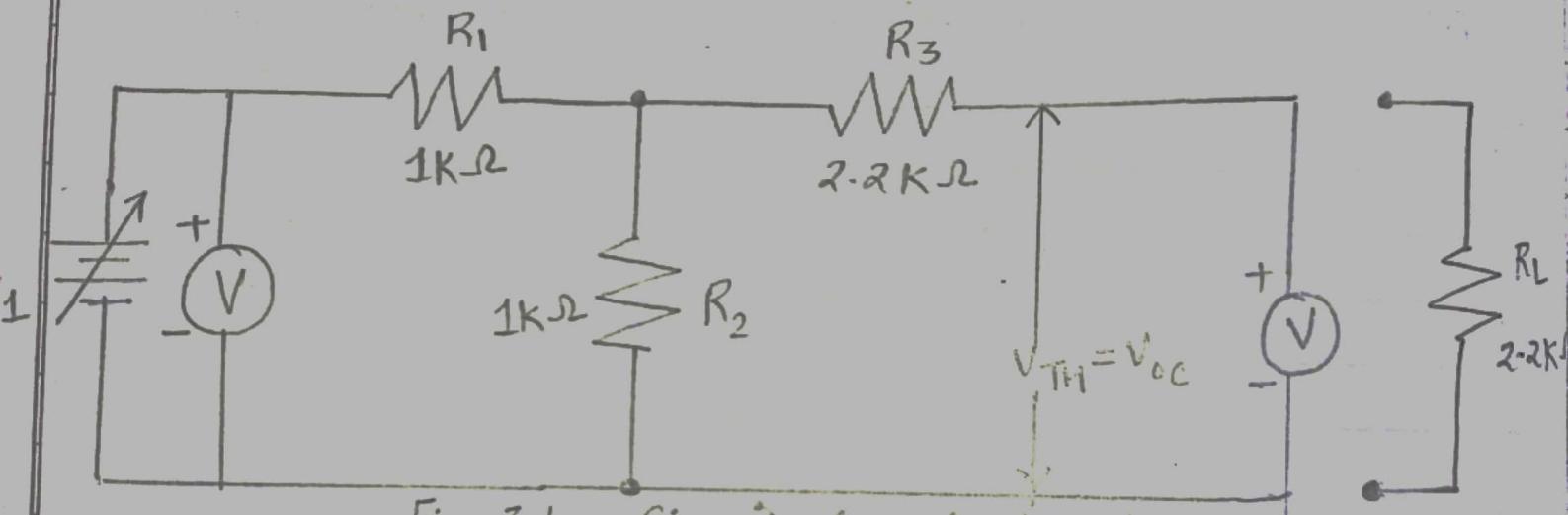


Fig 3-b Circuit for finding V_{TH}

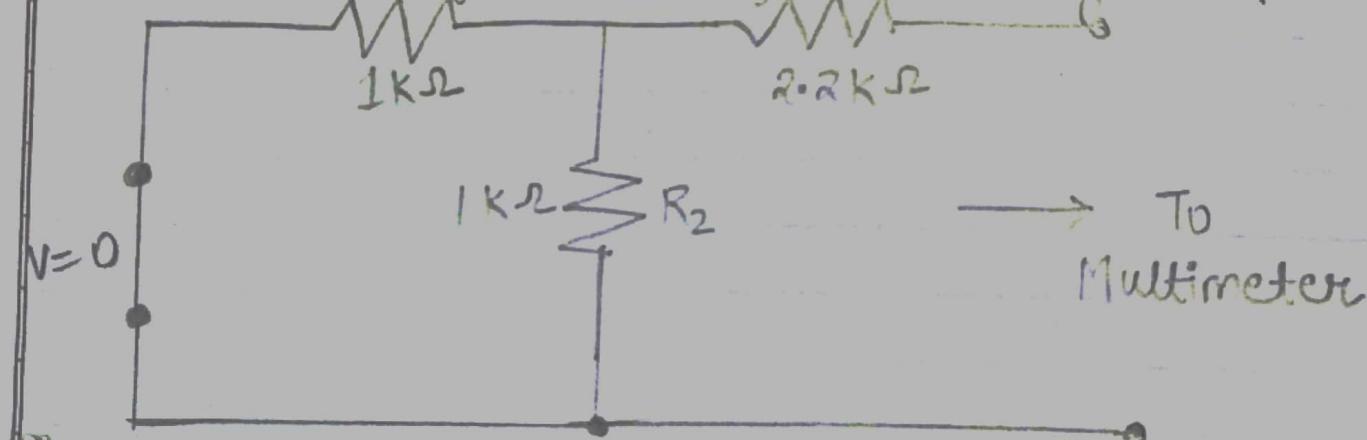

Circuit for finding R_{TH}

6. Measure I_L with connecting load at output terminals & compare with I'_L . Thevenin theorem states that $I_L = I'_L$

PRECAUTIONS


1. Connect the circuit elements as per the circuit diagram
 2. Avoid loose connections of the circuit elements
 3. Take the readings carefully and accurately
 4. Do not tamper the circuit elements.

OBSERVATIONS : Thevenin's Theorem

no	Input voltage (V)	V_{th} (V)	$R_{th}(LR)$	R_L (Ω)	I_L (mA)	I'_L (mA)	Error ($I_L - I'_L$) (mA)
1							
2							
3							
4							
5							
6							
7							
8							
9							
10							

RESULT: Thevenin Theorem has been verified at different voltage sources & resistances & corresponding errors are found.

Teacher's Signature.....

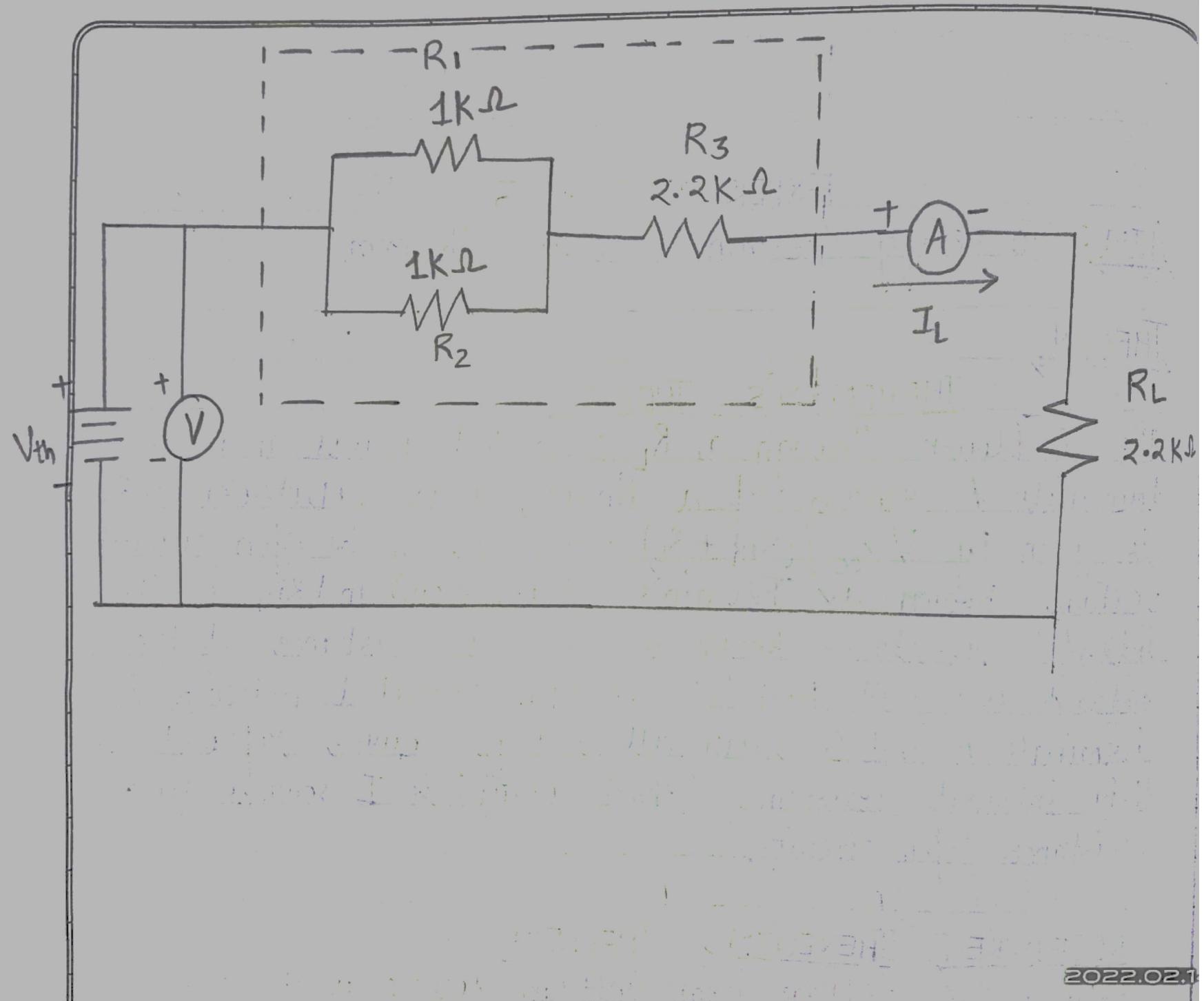

NORTON'S THEOREM

Any 2 terminals active network containing voltage sources & resistances when viewed from its output terminals is equivalent to a constant current source and a \parallel resistance. The $I_{\text{constant}} = I$ which would flow in a short circuit placed across the terminals and \parallel Resistance is the resistance of network when viewed from these open circuits terminal after all voltage & current sources have been removed & replaced by their internal resistance.

PROCEDURE : Norton's theorem

1. Apply DC voltage from voltage source to the input terminal of the network and measure the load current I_L at the output of the source.
2. Apply DC Voltage and measure short circuit I_{SC} by short circuiting load terminals.
3. Disconnecting the voltage source & load, short the input terminals of the network & measure the Norton's equivalent impedance R_N at the output terminals.
4. Draw Norton's equivalent circuits by connecting R_N in \parallel with I_{SC} .
5. Measure the load current I'_L with connecting load at output terminals and compare with I_L .

Norton's theorem states that $I_L = I'_L$

Teacher's Signature.....

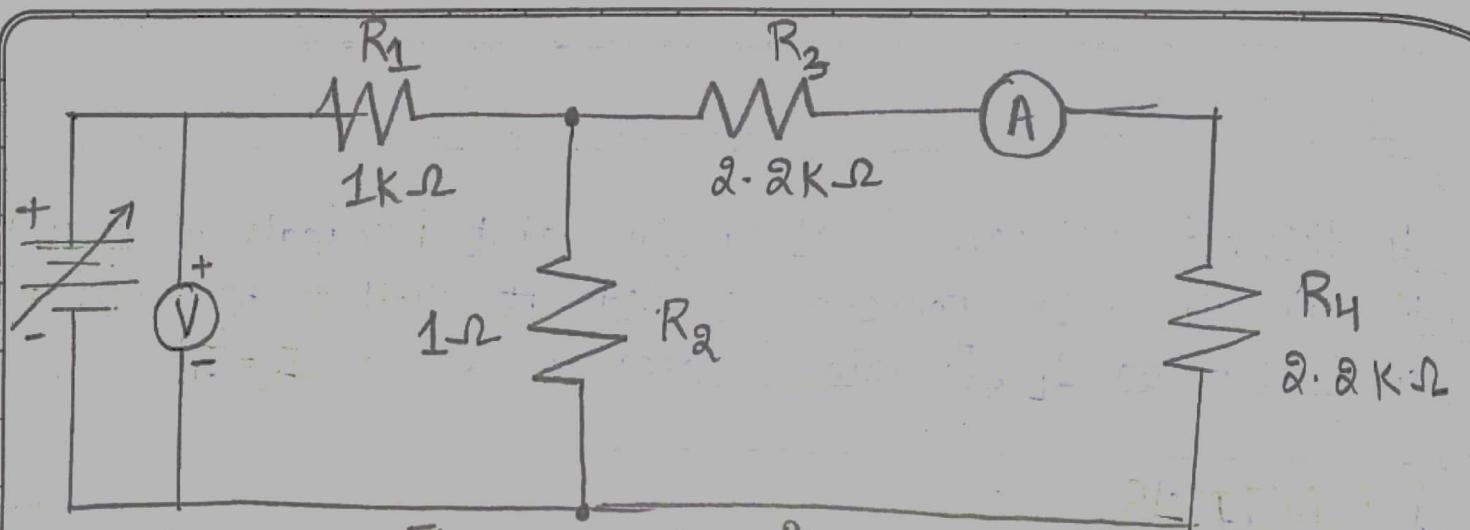


Fig 3-a Circuit to be Nortonize

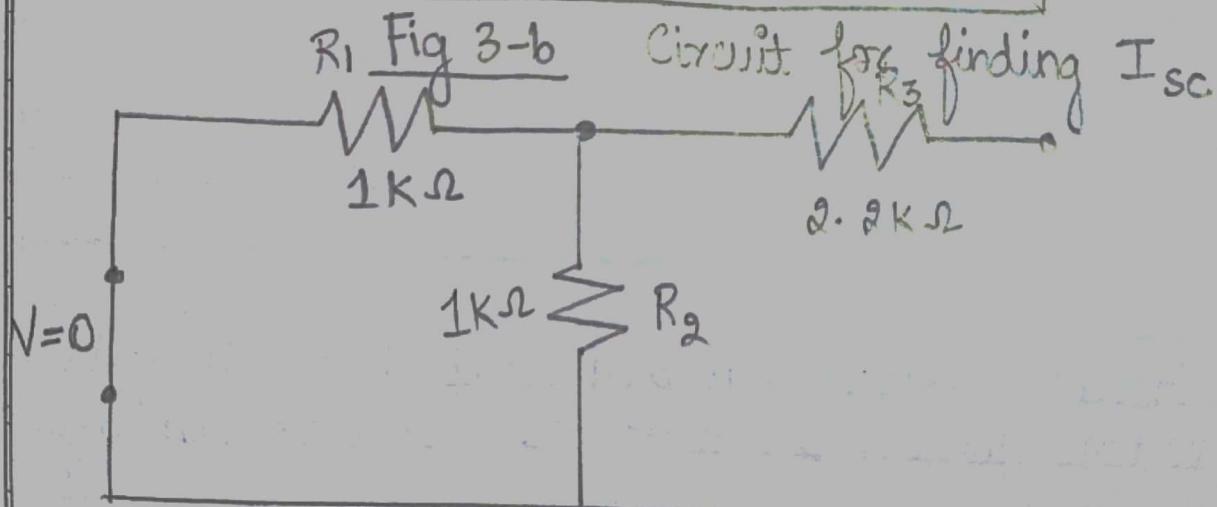
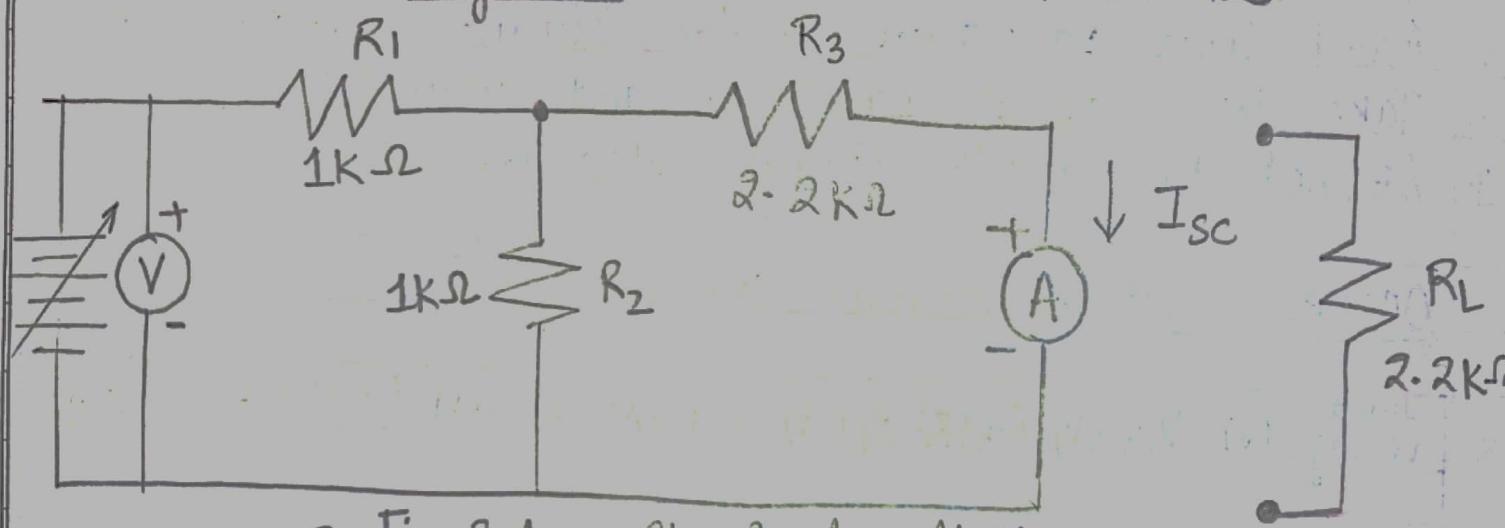


Fig 3-c : circuit for finding R_N

OBSERVATIONS

NORTON'S THEOREM

S.no	Input (V) Voltage	I_{sc} (mA)	R_N (Ω)	R_L (Ω)	I_L (mA)	I'_L (mA)	$\frac{\text{Error}}{(I_L - I'_L)} \times 100$ (%)
1							
2							
3							
4							
5							

RESULT: Norton's theorem has been verified for different current sources & resistances and corresponding errors are found.

EXPERIMENT NO. : 4

AIM: To verify superposition theorem and reciprocity theorem.

THEORY: SUPERPOSITION THEOREM

If any linear, bilateral network contains more than one source, then the current flowing through any branch is the sum of all currents, which would flow through that branch if each source were considered separately, and all the other sources being killed or deactivated. Short circuiting it can kill a voltage source & open circuiting it can kill a current.

PROCEDURE:

1. Connect V_1 & V_2 as shown in fig I-a.
2. For different V_1 & V_2 values note the DC ammeter reading as " I_T ".
3. Replace " V_2 " with a short circuit as shown in fig I-b & read the ammeter reading as " I_1 " for corresponding values of V_1 .
4. Replace " V_1 " with a short circuit as shown in fig I-c & connect " V_2 " in the circuit & read " I_2 " for corresponding values of V_2 .
5. $I_T = I_1 + I_2$

PRECAUTIONS :

1. Connect the circuit elements as per the circuit diagram.
2. Avoid loose connections of the circuit elements.
3. Take the readings carefully & accurately.
4. Do not tamper the circuit elements.

Teacher's Signature.....

Fig I-a

Circuit considered for v₁ of SPT



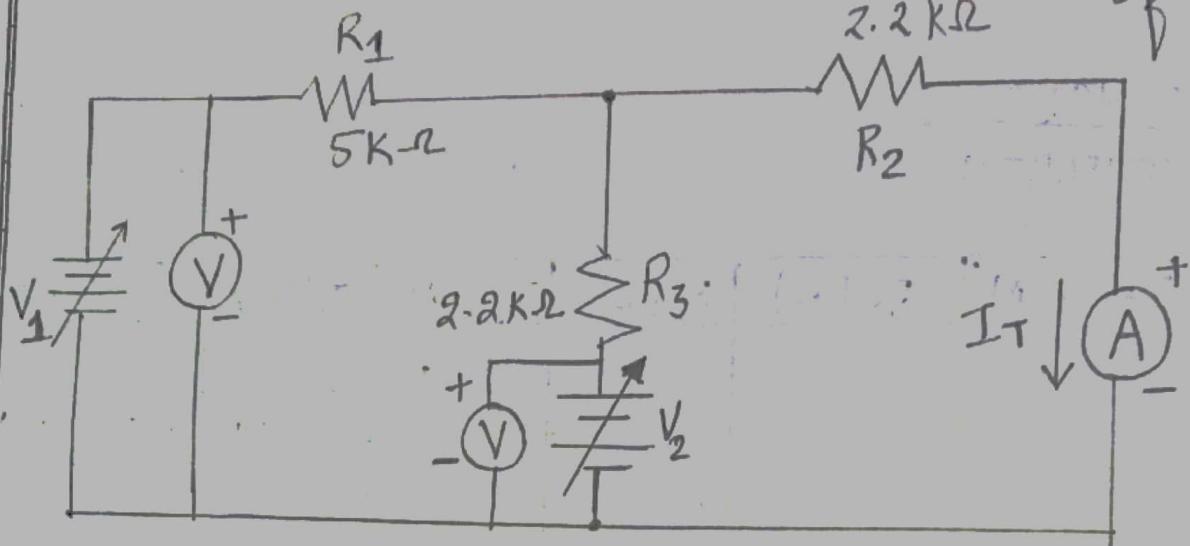


Fig - I-b

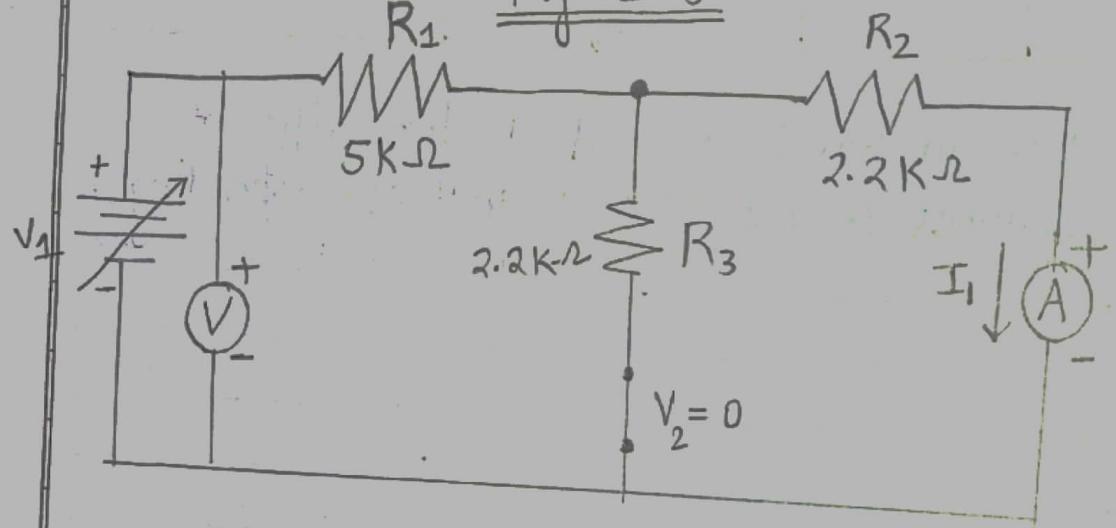

Circuit with
 V_1 only

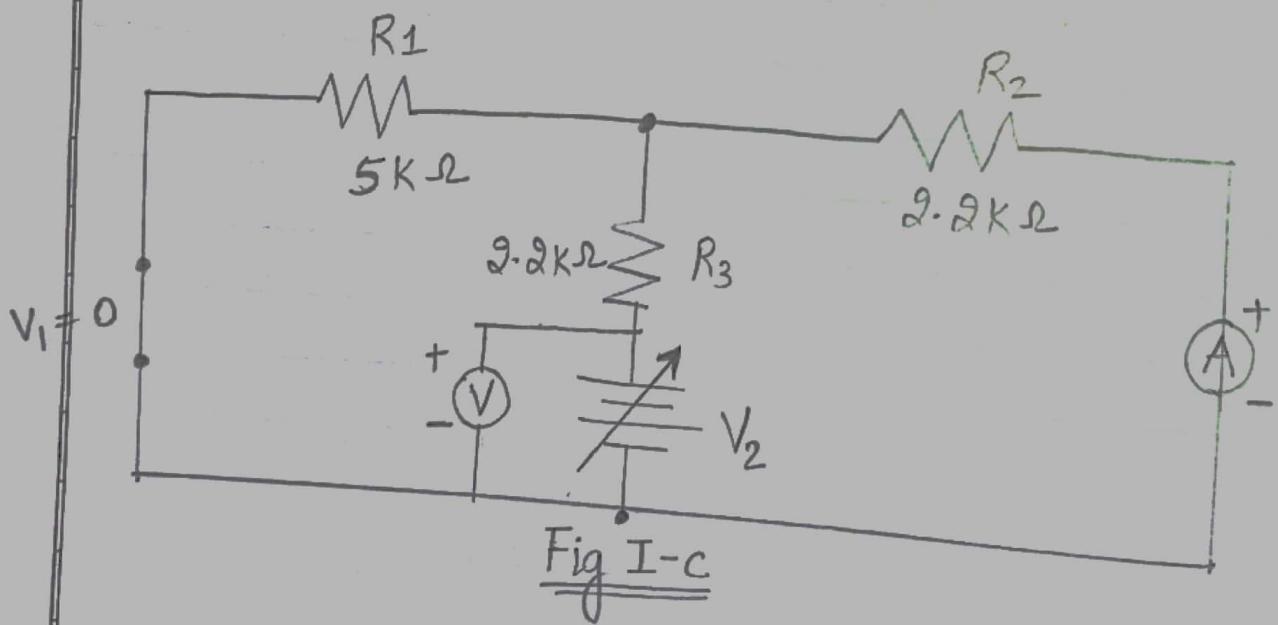

Circuit with
 V_2 only

Fig I-c

RESULT:

Superposition theorem has been verified for different voltage sources & corresponding errors are found.

THEORY:RECIPROCITY THEOREM

In any linear bilateral network, if a source of emf E in first branch produces a current I_1 in second branch, then the same emf E acting in the second branch would produce the same current I_1 in first branch.

PROCEDURE:

1. Connect the circuit as shown in fig I-d.
2. Apply some voltage V .
3. Note down the ammeter readings as " I_1 ".
4. Interchange the ammeter & voltage source as shown in fig I-e and read the ammeter reading as " I_2 ".
5. Repeat the above procedure for different values of V and tabulate the values.
6. I_1 should be equal to I_2 .

PRECAUTIONS:

1. Connect the circuit elements as per the diagram.
2. Avoid loose connections of the circuit elements.
3. Take the readings carefully & accurately.

Teacher's Signature.....

Superposition Theorem

OBSERVATION TABLE

S.no	Input voltage V_1 (volt)	Input voltage V_2 (volt)	I_1 (mA)	I_2 (mA)	I_3 (mA)	Error $\frac{I_1}{I_1 + I_2}$
1	1.00	0.00	0.00	0.00	0.00	0.00%
2	1.00	0.50	0.00	0.00	0.00	0.00%
3	1.00	1.00	0.00	0.00	0.00	0.00%
4	1.00	1.50	0.00	0.00	0.00	0.00%
5	1.00	2.00	0.00	0.00	0.00	0.00%

4. Do not tamper the circuit elements

RESULT:

Reciprocity theorem has been verified for different voltage sources & corresponding errors are found.

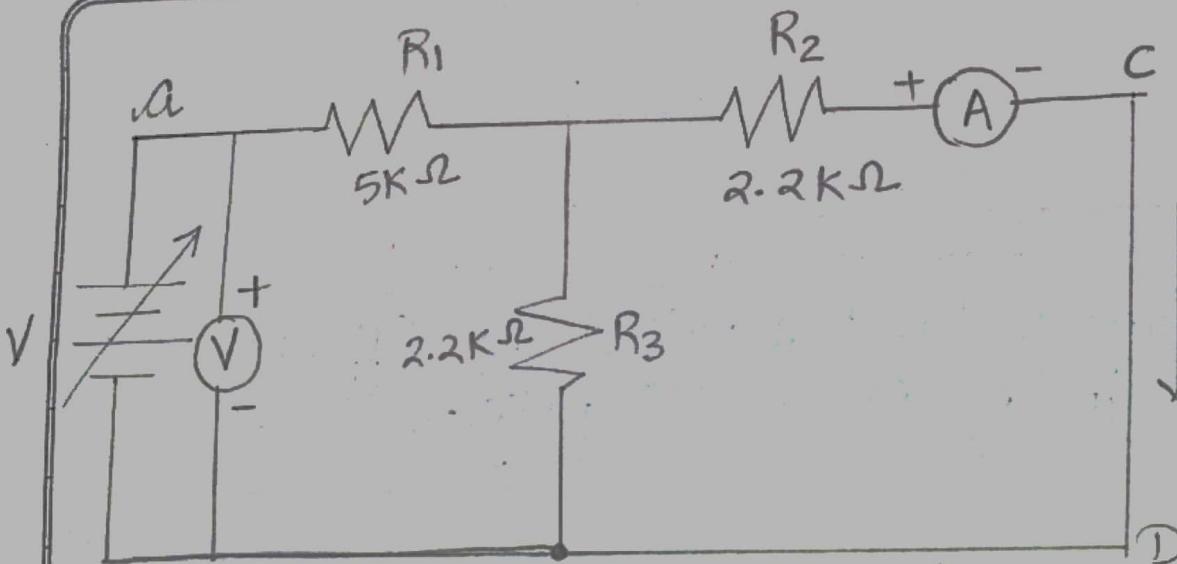


Fig I-d : circuit for finding I_1

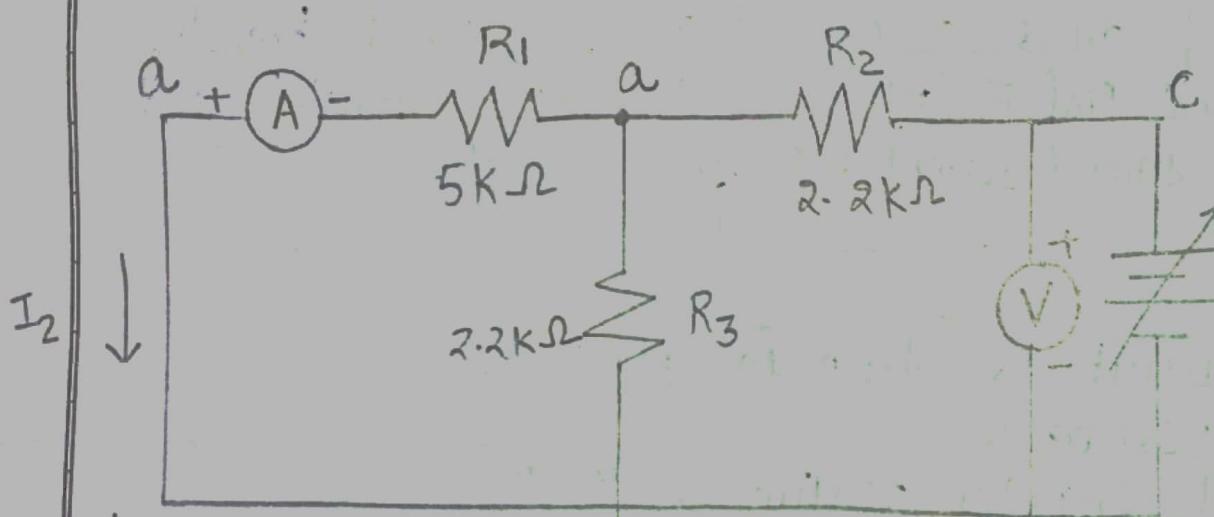


Fig I-d : Circuit for finding I_2

OBSERVATION TABLE : Reciprocity Theorem

S.no	Input voltage V (volts)	I_1 (mA)	I_2 (mA)	Error $(I_1 - I_2)$ mA

AIM: To verify maximum power transfer theory.

THEORY:

It states that in a D.C. Network maximum power is transferred from source to the load when the $R_L = \text{source resistance}$. The source resistance is the internal resistance of the network as viewed from the load terminals.

The maximum power transferred when $R_S = R_L$ is

$$P_{\max} = V^2 / R_L$$

PROCEDURE:

1. Connect the circuit as shown in fig 5-a.
2. Varying the load resistance in steps & note the ammeter readings & calculate power.
3. Plot the graph by taking resistance on x-axis and power on y-axis.
4. R_S should be equal to R_L for maximum power transfer.



PRECAUTIONS:

1. Connect the circuit elements as per the circuit diagram.
2. Avoid loose connections of the circuit elements.
3. Take the readings carefully & accurately.
4. Do not tamper the circuit elements.

RESULT:

$$P = P_{\max} \text{ when } R_S = R_L$$

Teacher's Signature.....

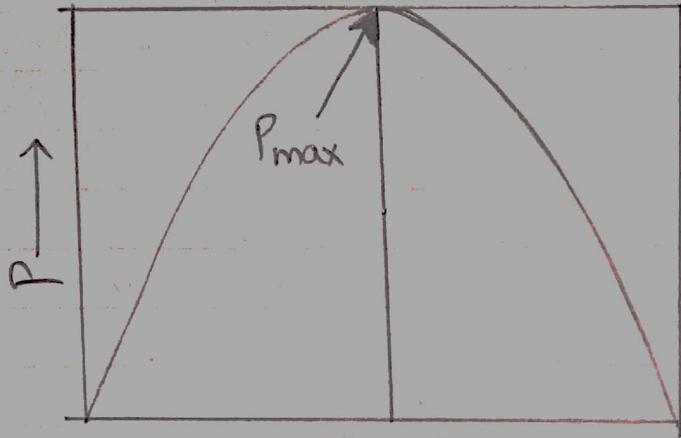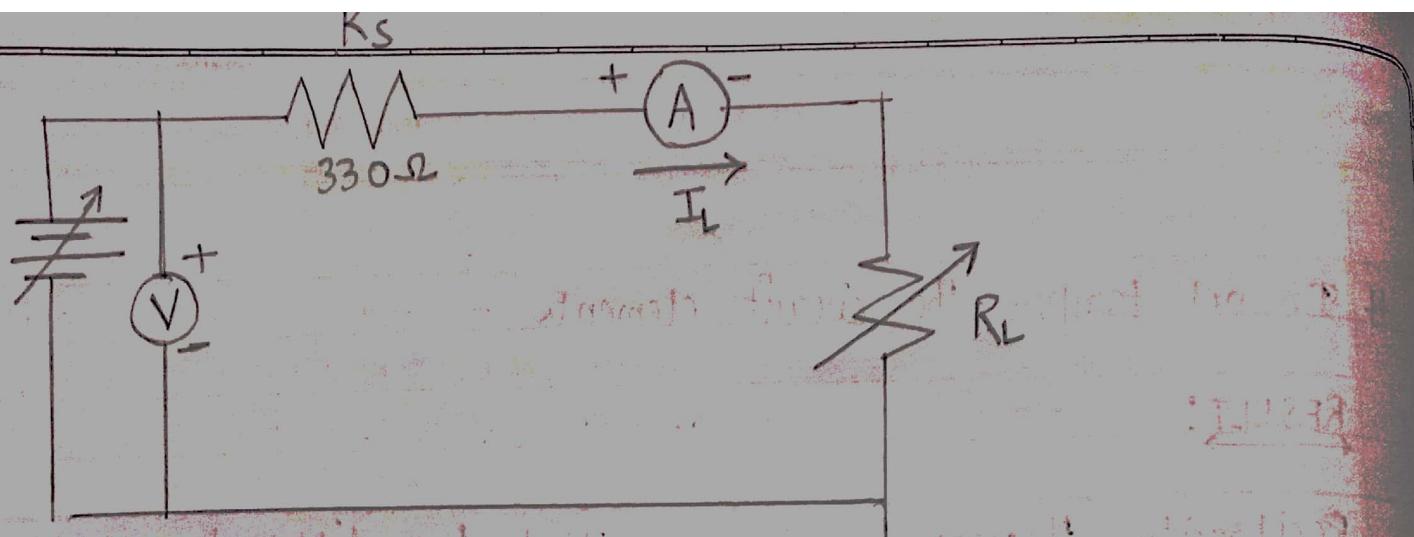

$$R_s = R_L$$

OBSERVATIONS:

S.no	Input voltage V (Volts)	$R_s (\Omega)$ Series resistance	$R_L (\Omega + \epsilon)$ Load resistance	I_L (mA) Load current	$P = I^2 R$ R_L Load Power


ELECTRICAL EXPERIMENT NO. : 6

AIM: To measure the power & power factor by 3 voltmeter and 3 ammeter method.

APPARATUS: AC Voltmeter, AC supply, Circuit Board, Connecting wires

THEORY: THREE VOLTMETER METHOD

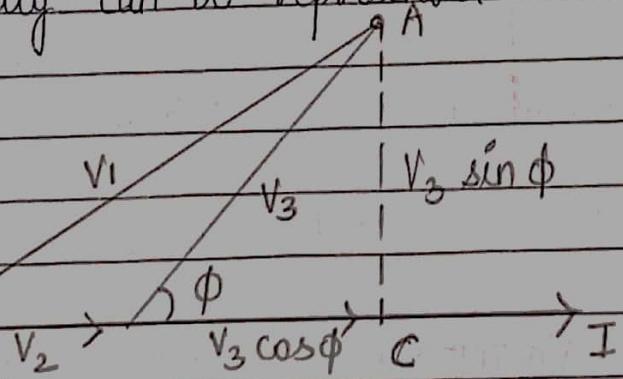On analysing the given circuit it is observed that the two elements, resistor & inductor are connected in series i.e. the same amount of current is passing through each element. The voltage drop in inductor is leading the current which is graphically can be represented as



PROCEDURE:

1. Give the connections as in the circuit diagram
2. Apply 230 V, 1-φ AC voltage by means of 1-φ A varies to the series combination of choke coil & external resistance.
3. Note down the readings of the 3 voltmeters.
4. Apply different voltages in suitable steps and note down the readings of voltmeter.

Teacher's Signature.....

5. Calculate Power and Power Factor of coil using the formulae given below.

Now, from figure, Apply Pythagoras theorem on ΔABC .

$$V_1^2 = (V_2 + V_3 \cos \phi)^2 + (V_3 \sin \phi)^2$$

$$V_1^2 = V_2^2 + 2V_2 V_3 \cos \phi + V_3^2 \cos^2 \phi + V_3^2 \sin^2 \phi$$

$$V_1^2 - V_2^2 - V_3^2 = 2V_2 V_3 \cos \phi$$

$$\cos \phi = (V_1^2 - V_2^2 - V_3^2) / 2V_2 V_3 \quad \text{--- (1)}$$

For real Power :-

$$2V_2 V_3 \cos \phi = V_1^2 - V_2^2 - V_3^2$$

$$2(IR) V_3 \cos \phi = V_1^2 - V_2^2 - V_3^2$$


$$V_3 I \cos \phi = (V_1^2 - V_2^2 - V_3^2) / 2R$$

$$\text{Real Power} = (V_1^2 - V_2^2 - V_3^2) / 2R \quad \text{--- (2)}$$

Sno	I	V_1	V_2	V_3	Power	Power Factor

Teacher's Signature.....

CIRCUIT DIAGRAM

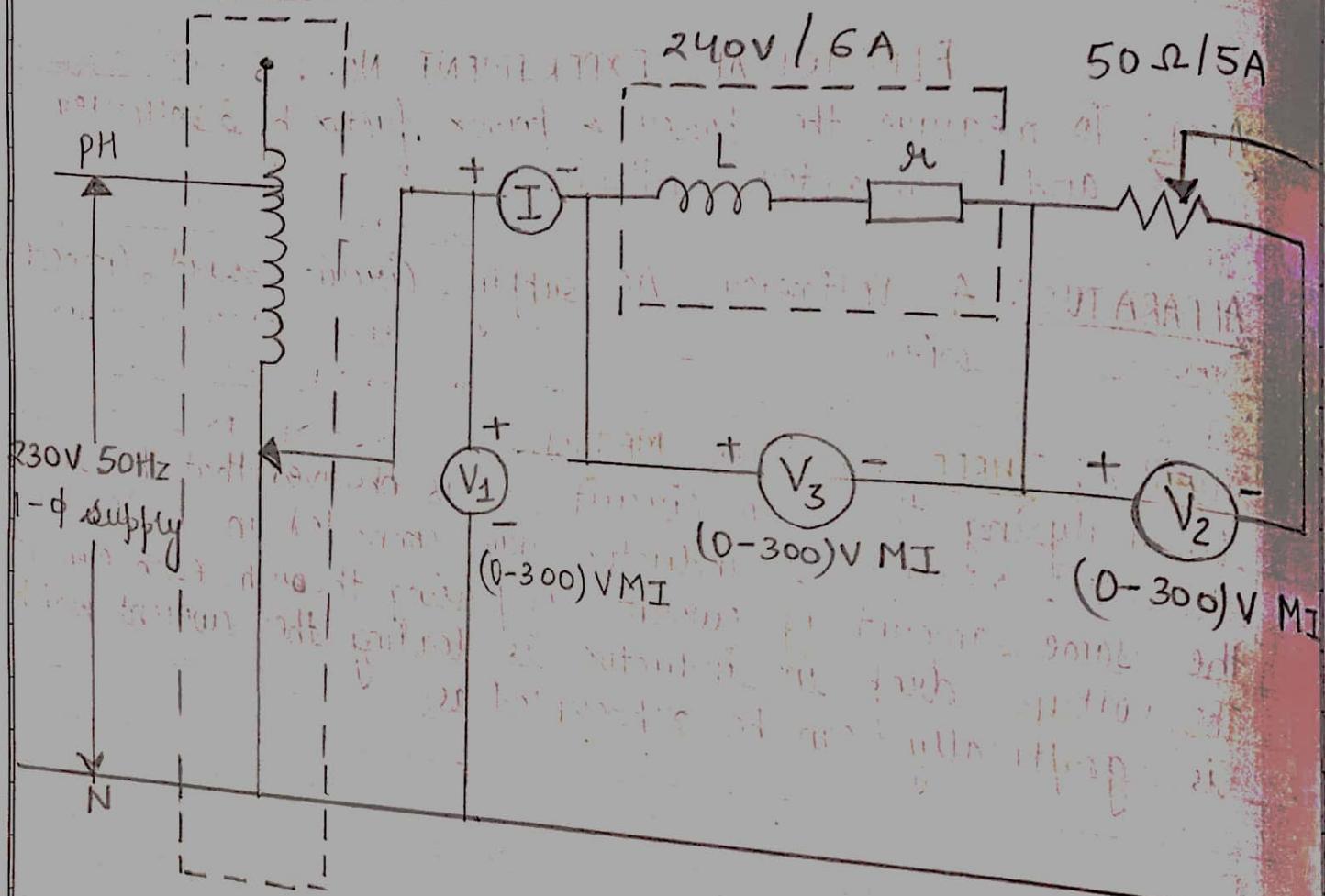


THREE VOLTmeter METHOD

THEORY: THREE AMMETER METHOD

On analysing the given circuit, the total current I_1 is divided into I_2 & I_3 . I_2 current is passing through resistor therefore it is in phase with applied voltage, while I_3 is passing through inductor therefore it is lagged by angle ϕ wrt applied voltage.

PHASOR DIAGRAM

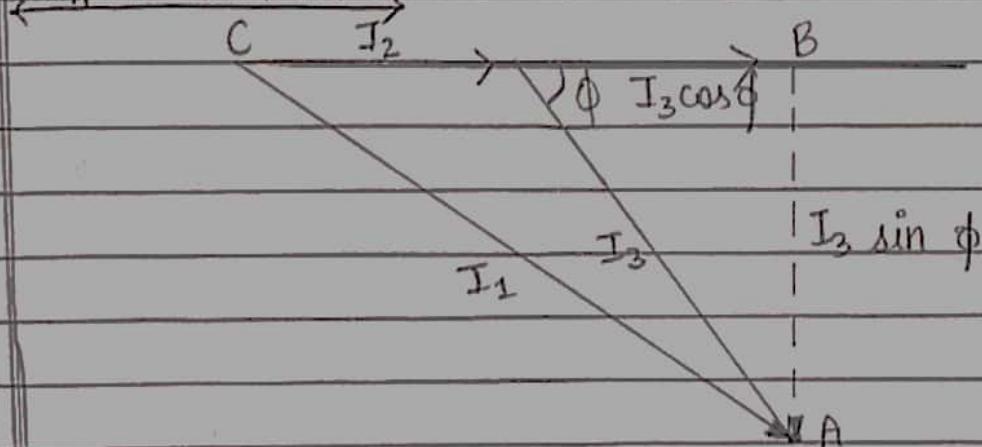


PROCEDURE

1. Give the connections as in the circuit diagram.
2. Apply 230V, 1-φ AC voltage by means of 1-φ AC variac to the series combination of choke coil & external resistance.
3. Note down the readings of all the three ammeters.
4. Now vary the rheostat ($50\Omega/5A$) so that I_1 varies in suitable steps.
5. At each step tabulate the reading of the three ammeters.
6. Calculate Power & Power Factor of coil using the formulae given below

Resolve I into components & consider $\triangle ABC$

Teacher's Signature.....

1- ϕ variant
240V / (0-270V)

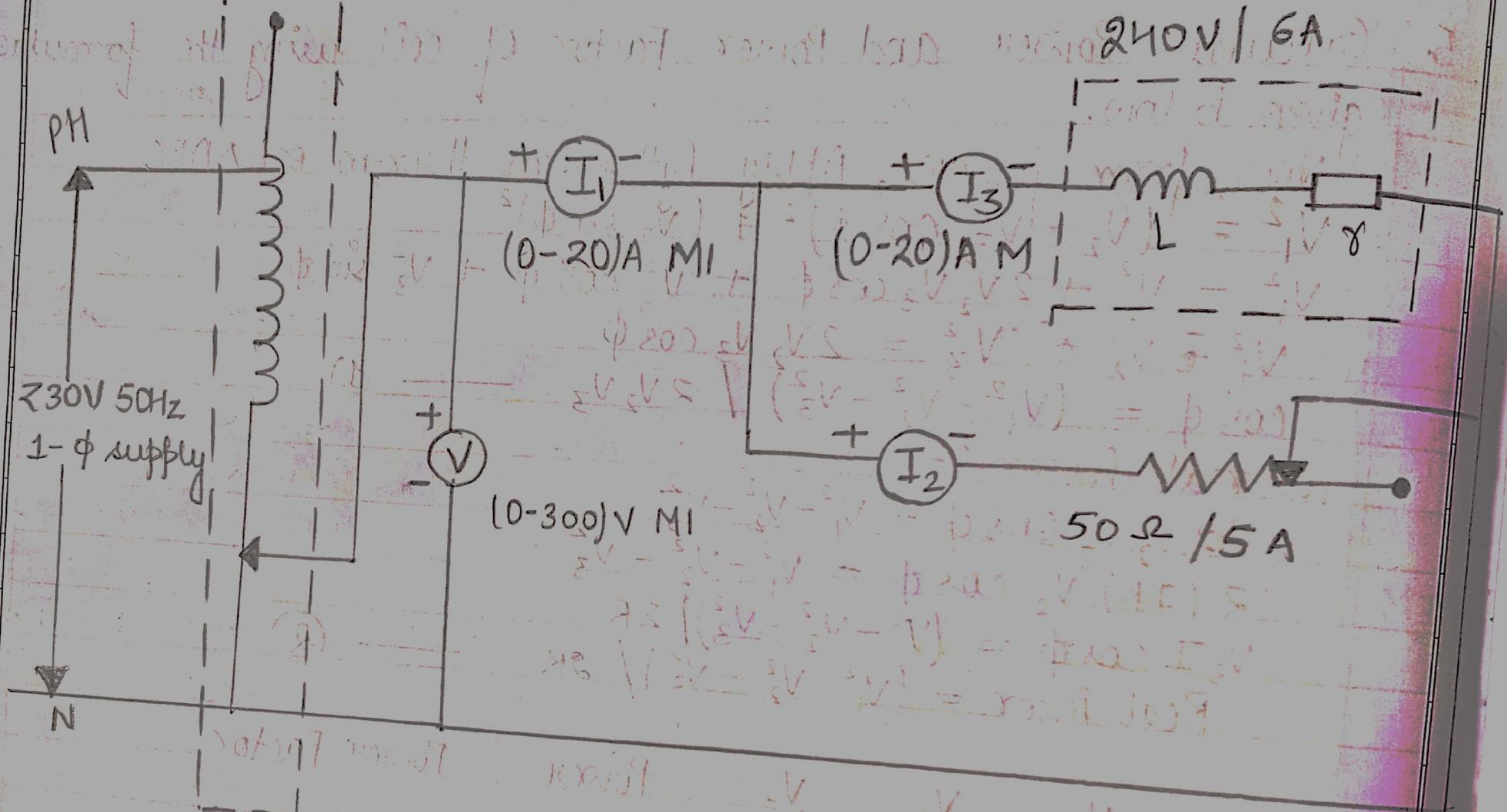

THREE AMMETER METHOD

$$(I_1)^2 = (I_2 + I_3 \cos\phi)^2 + (I_3 \sin\phi)^2$$

$$I_1^2 = I_2^2 + I_3^2 \cos^2\phi + 2I_2 I_3 \cos\phi + I_3^2 \sin^2\phi$$

$$I_1^2 = I_2^2 + I_3^2 + 2I_2 I_3 \cos\phi$$

$$I_1^2 - I_2^2 - I_3^2 = 2I_2 I_3 \cos\phi$$

$$\text{Now, } \cos\phi = (I_1^2 - I_2^2 - I_3^2) / 2I_2 I_3$$

Now, consider above equation again.

$$2I_2 I_3 \cos\phi = (I_1^2 - I_2^2 - I_3^2)$$

$$2(V/R) I_3 \cos\phi = (I_1^2 - I_2^2 - I_3^2)$$

$$VI_3 \cos\phi = (I_1^2 - I_2^2 - I_3^2) R/2$$

$$P = (I_1^2 - I_2^2 - I_3^2) R/2$$

$$\text{Real Power} = (I_1^2 - I_2^2 - I_3^2) R/2$$

S.no	V	I_1	I_2	I_3	P	$\cos\phi$

RESULT:

Power & Power factor of load (coil) for different AC voltage sources & load (coil) combination has been successfully calculated by three voltmeter & three ammeter method.